

Logic Design

Tutorial 4

Amr Keleg

Faculty of Engineering, Ain Shams University

August 7, 2020

Contact: amr_mohamed@live.com

Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code

Outline

1 Logic gates

■ Motivation

- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2



Buffer
 $F = A$

A	F
0	0
1	1



AND
 $F = AB$

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1



OR
 $F = A+B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1



XOR
 $F = A \oplus B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0



NAND
 $F = \overline{AB}$

A	F
0	1
1	0



NAND
 $F = \overline{AB}$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0



NOR
 $F = \overline{A+B}$


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0




XNOR
 $F = \overline{A \oplus B}$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

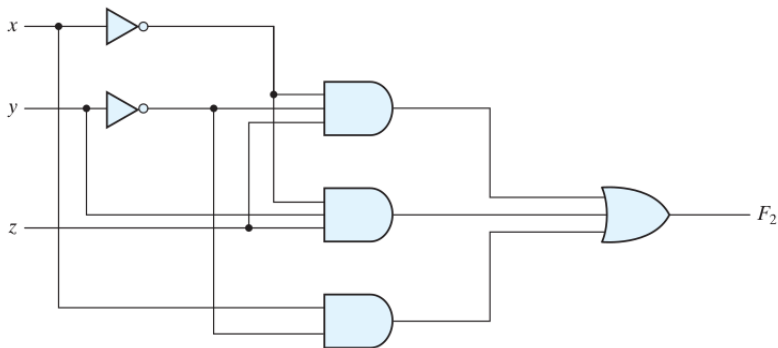What is the output of this circuit for the following input $X=0$, $Y=0$, $Z=1$?



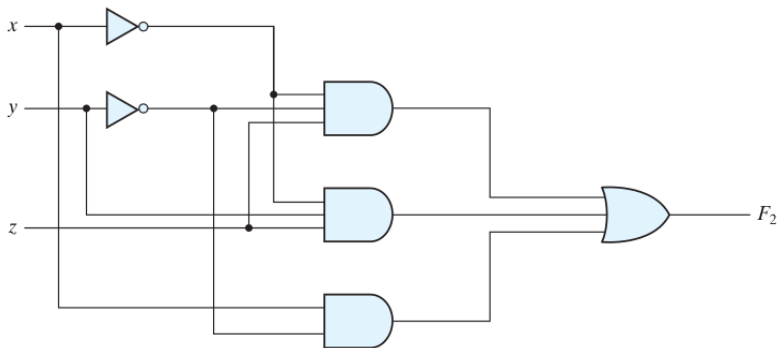What is the output of this circuit for the following input $X=0$, $Y=0$, $Z=1$?




$$F_2 = \bar{X}.\bar{Y}.Z + \bar{X}.Y.Z + X.\bar{Y}$$

Using Boolean Algebra, we can simplify the function to

$$F2 = X.\overline{Y} + \overline{X}.Z$$

Using Boolean Algebra, we can simplify the function to
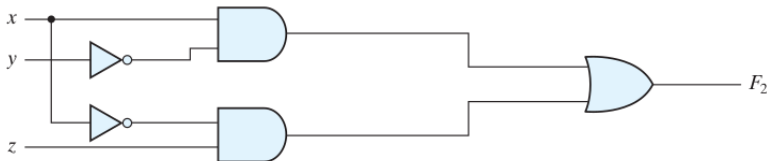
$$F_2 = X.\overline{Y} + \overline{X}.Z$$


Outline

1 Logic gates

- Motivation

- Axioms of Boolean Algebra

- Sheet 3 - Question 4

- Sheet 3 - Question 7

- Sheet 3 - Question 9

- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2

Table 2.1*Postulates and Theorems of Boolean Algebra*

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

How to prove something like $X + (Y + Z) = (X + Y) + Z$?

How to prove something like $X + (Y + Z) = (X + Y) + Z$?

Using Truth Table:

X	Y	Z	$(Y+Z)$	$X + (Y+Z)$	$(X+Y)$	$(X+Y) + Z$
0	0	0	0	0	0	0
0	0	1	1	1	0	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

I will wear a jacket ($Jacket$) if:

- It rains ($RAIN$)
- It doesn't rain (\overline{RAIN}) and it's cold ($COLD$)

$Jacket =$

I will wear a jacket ($Jacket$) if:

- It rains ($RAIN$)
- It doesn't rain (\overline{RAIN}) and it's cold ($COLD$)

$Jacket =$

$$RAIN + \overline{RAIN}.COLD =$$

I will wear a jacket (*Jacket*) if:

- It rains (*RAIN*)
- It doesn't rain (\overline{RAIN}) and it's cold (*COLD*)

Jacket =

$RAIN + \overline{RAIN}.COLD =$

$RAIN + COLD$

I will wear a jacket (*Jacket*) if:

- It rains (*RAIN*)
- It doesn't rain (\overline{RAIN}) and it's cold (*COLD*)

$$\begin{aligned} Jacket &= \\ RAIN + \overline{RAIN}.COLD &= \\ RAIN + COLD \end{aligned}$$

Generally: $X + \overline{X}.Y = X + Y$

I will wear a jacket (*Jacket*) if:

- It rains (*RAIN*)
- It doesn't rain (\overline{RAIN}) and it's cold (*COLD*)

Jacket =

$$RAIN + \overline{RAIN}.COLD =$$

$$RAIN + COLD$$

Generally: $X + \overline{X}.Y = X + Y$

$$\text{AND } \overline{X} + X.Y = \overline{X} + Y$$

Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2

Simplify the following equations:

- c) $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$ (to one literal)

Simplify the following equations:

■ c) $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$ (to one literal)
 $= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD$

Simplify the following equations:

$$\begin{aligned} \blacksquare \text{ c) } & \overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD) \text{ (to one literal)} \\ &= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD \\ &= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB \end{aligned}$$

Simplify the following equations:

- c) $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$ (to one literal)
$$= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD$$
$$= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB$$
$$= \overline{A}B(\overline{D} + D \cdot (\overline{C} + C)) + AB$$

Simplify the following equations:

$$\begin{aligned} \blacksquare \text{ c) } & \overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD) \text{ (to one literal)} \\ &= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD \\ &= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB \\ &= \overline{A}B(\overline{D} + D \cdot (\overline{C} + C)) + AB \\ &= \overline{A}B(\overline{D} + D) + AB \end{aligned}$$

Simplify the following equations:

$$\begin{aligned} \blacksquare \text{ c) } & \overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD) \text{ (to one literal)} \\ &= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD \\ &= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB \\ &= \overline{A}B(\overline{D} + D \cdot (\overline{C} + C)) + AB \\ &= \overline{A}B(\overline{D} + D) + AB \\ &= \overline{A}B + AB \end{aligned}$$

Simplify the following equations:

$$\begin{aligned} \blacksquare \text{ c) } & \overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD) \text{ (to one literal)} \\ &= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD \\ &= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB \\ &= \overline{A}B(\overline{D} + D \cdot (\overline{C} + C)) + AB \\ &= \overline{A}B(\overline{D} + D) + AB \\ &= \overline{A}B + AB \\ &= B(\overline{A} + A) \end{aligned}$$

Simplify the following equations:

$$\begin{aligned} \blacksquare \text{ c) } & \overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD) \text{ (to one literal)} \\ &= \overline{A}B\overline{D} + \overline{A}B\overline{C}D + AB + \overline{A}BCD \\ &= \overline{A}B(\overline{D} + \overline{C}D + CD) + AB \\ &= \overline{A}B(\overline{D} + D \cdot (\overline{C} + C)) + AB \\ &= \overline{A}B(\overline{D} + D) + AB \\ &= \overline{A}B + AB \\ &= B(\overline{A} + A) \\ &= B \end{aligned}$$

Simplify the following equations:

■ a) $\overline{A}\overline{C} + ABC + A\overline{C}$ (to three literals) =

Simplify the following equations:

■ a) $\overline{A}\overline{C} + ABC + A\overline{C}$ (to three literals) =
 $\overline{C} \cdot (\overline{A} + A) + ABC =$

Simplify the following equations:

■ a) $\overline{A}\overline{C} + ABC + A\overline{C}$ (to three literals) =
 $\overline{C}.\overline{A} + A + ABC =$
 $\overline{C}.(1) + ABC =$

Simplify the following equations:

■ a) $\overline{A}\overline{C} + ABC + A\overline{C}$ (to three literals) =
 $\overline{C}(\overline{A} + A) + ABC =$
 $\overline{C}(1) + ABC =$
 $\overline{C} + ABC =$

Simplify the following equations:

■ a) $\overline{A}\overline{C} + ABC + A\overline{C}$ (to three literals) =
 $\overline{C}.\overline{A} + A + ABC =$
 $\overline{C} + ABC =$
 $\overline{C} + AB$

Simplify the following equations:

- e) $AB\overline{C}D + \overline{A}BD + ABCD$ (to two literals)

Simplify the following equations:

■ e) $AB\overline{C}D + \overline{A}BD + ABCD$ (to two literals)
 $= BD(\overline{A}\overline{C} + \overline{A} + AC)$

Simplify the following equations:

- e) $AB\overline{C}D + \overline{A}BD + ABCD$ (to two literals)
 $= BD(\overline{A}\overline{C} + \overline{A} + AC)$
 $= BD(A(\overline{C} + C) + \overline{A})$

Simplify the following equations:

- e) $AB\bar{C}D + \bar{A}BD + ABCD$ (to two literals)
 $= BD(A\bar{C} + \bar{A} + AC)$
 $= BD(A(\bar{C} + C) + \bar{A})$
 $= BD(A + \bar{A})$

Simplify the following equations:

- e) $AB\bar{C}D + \bar{A}BD + ABCD$ (to two literals)
 $= BD(A\bar{C} + \bar{A} + AC)$
 $= BD(A(\bar{C} + C) + \bar{A})$
 $= BD(A + \bar{A})$
 $= BD$

Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- **Sheet 3 - Question 7**
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code


- Sheet 2 - Question 2

Draw logic diagrams of the circuits that implement the original and simplified expressions in Problem 2.4

c) $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$ and B

Draw logic diagrams of the circuits that implement the original and simplified expressions in Problem 2.4

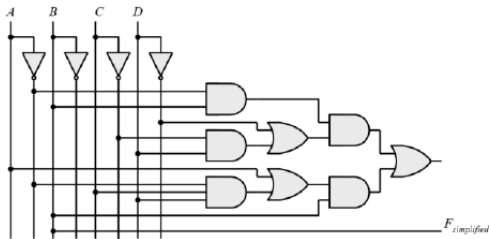c) $\overline{A}B(\overline{D} + \overline{C}D) + B(A + \overline{A}CD)$ and B



Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- **Sheet 3 - Question 9**
- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\text{Complement} = \overline{(X\overline{Y} + \overline{X}Y)}$$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\begin{aligned}\text{Complement} &= \overline{(X\overline{Y} + \overline{X}Y)} \\ &= \overline{(X\overline{Y})} \cdot \overline{(\overline{X}Y)}\end{aligned}$$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\text{Complement} = \overline{(X\overline{Y} + \overline{X}Y)}$$

$$= \overline{(X\overline{Y})} \cdot \overline{(\overline{X}Y)}$$

$$= (\overline{X} + Y) \cdot (X + \overline{Y})$$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\text{Complement} = \overline{(X\overline{Y} + \overline{X}Y)}$$

$$= \overline{(X\overline{Y})} \cdot \overline{(\overline{X}Y)}$$

$$= (\overline{X} + Y) \cdot (X + \overline{Y})$$

$$= (\overline{X}X + \overline{X}\overline{Y} + YX + Y\overline{Y})$$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\text{Complement} = \overline{(X\overline{Y} + \overline{X}Y)}$$

$$= \overline{(X\overline{Y})} \cdot \overline{(\overline{X}Y)}$$

$$= (\overline{X} + Y) \cdot (X + \overline{Y})$$

$$= (\overline{X}X + \overline{X}\overline{Y} + YX + Y\overline{Y})$$

$$= (0 + \overline{X}\overline{Y} + XY + 0)$$

Find the complement of the following expressions:

■ a) $X\overline{Y} + \overline{X}Y$

$$\text{Complement} = \overline{(X\overline{Y} + \overline{X}Y)}$$

$$= \overline{(X\overline{Y})} \cdot \overline{(\overline{X}Y)}$$

$$= (\overline{X} + Y) \cdot (X + \overline{Y})$$

$$= (\overline{X}X + \overline{X}\overline{Y} + YX + Y\overline{Y})$$

$$= (0 + \overline{X}\overline{Y} + XY + 0)$$

$$= (\overline{X}\overline{Y} + XY)$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\text{Complement} = \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})}$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\begin{aligned}\text{Complement} &= \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})} \\ &= \overline{((a + c).(a + \bar{b})) . (\bar{a} + b + \bar{c})}\end{aligned}$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\text{Complement} = \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b})) . (\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b}))} + \overline{(\bar{a} + b + \bar{c})}$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\text{Complement} = \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b})) . (\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b}))} + \overline{(\bar{a} + b + \bar{c})}$$

$$= \overline{(a + c)} + \overline{(a + \bar{b})} + \overline{(\bar{a} + b + \bar{c})}$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\text{Complement} = \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b})) . (\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b}))} + \overline{(\bar{a} + b + \bar{c})}$$

$$= \overline{(a + c)} + \overline{(a + \bar{b})} + \overline{(\bar{a} + b + \bar{c})}$$

$$= \bar{a}\bar{c} + \bar{a}b + a\bar{b}c$$

Find the complement of the following expressions:

■ b) $(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$

$$\text{Complement} = \overline{(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b})) . (\bar{a} + b + \bar{c})}$$

$$= \overline{((a + c).(a + \bar{b}))} + \overline{(\bar{a} + b + \bar{c})}$$

$$= \overline{(a + c)} + \overline{(a + \bar{b})} + \overline{(\bar{a} + b + \bar{c})}$$

$$= \bar{a}\bar{c} + \bar{a}b + a\bar{b}c$$

Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2

15* Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals:

<i>A</i>	<i>B</i>	<i>C</i>	<i>T</i>₁	<i>T</i>₂
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

15* Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals:

<i>A</i>	<i>B</i>	<i>C</i>	<i>T</i>₁	<i>T</i>₂
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$T_1 = ?$

15* Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals:

<i>A</i>	<i>B</i>	<i>C</i>	<i>T</i>₁	<i>T</i>₂
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

15* Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals:

A	B	C	T_1	T_2
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$T_1 = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C}$$

$$T1 = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C}$$

$$\begin{aligned}T1 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} \\ &= \overline{A}\overline{C}(\overline{B} + B) + \overline{A}\overline{B}C\end{aligned}$$

$$\begin{aligned}T1 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} \\&= \overline{A}\overline{C}(\overline{B} + B) + \overline{A}\overline{B}C \\&= \overline{A}\overline{C} + \overline{A}\overline{B}C\end{aligned}$$

$$\begin{aligned}T1 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} \\&= \overline{A}\overline{C}(\overline{B} + B) + \overline{A}\overline{B}C \\&= \overline{A}\overline{C} + \overline{A}\overline{B}C \\&= \overline{A}(\overline{C} + \overline{B}C)\end{aligned}$$

$$\begin{aligned}T1 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} \\&= \overline{A}\overline{C}(\overline{B} + B) + \overline{A}\overline{B}C \\&= \overline{A}\overline{C} + \overline{A}\overline{B}C \\&= \overline{A}(\overline{C} + \overline{B}C) \\&= \overline{A}(\overline{C} + \overline{B})\end{aligned}$$

$$\begin{aligned}T1 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} \\&= \overline{A}\overline{C}(\overline{B} + B) + \overline{A}\overline{B}C \\&= \overline{A}\overline{C} + \overline{A}\overline{B}C \\&= \overline{A}(\overline{C} + \overline{B}C) \\&= \overline{A}(\overline{C} + \overline{B}) \\&= \overline{A}(\overline{B} + \overline{C})\end{aligned}$$

15* Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals:

<i>A</i>	<i>B</i>	<i>C</i>	<i>T</i>₁	<i>T</i>₂
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$T_2 = ?$

$$T2 = \overline{T1} = \overline{A(\overline{B} + \overline{C})}$$

$$T2 = \overline{T1} = \overline{\overline{A}(\overline{B} + \overline{C})} = A + BC$$

Outline

1 Logic gates

2 Gray code

■ Sheet 2 - Question 2

Outline

1 Logic gates

- Motivation
- Axioms of Boolean Algebra
- Sheet 3 - Question 4
- Sheet 3 - Question 7
- Sheet 3 - Question 9
- Sheet 3 - Question 15

2 Gray code

- Sheet 2 - Question 2

Q2) Write an algorithm for converting from binary to gray code.
You can draw a flow chart.

Q2) Write an algorithm for converting from binary to gray code.
You can draw a flow chart.

Index	3	2	1	0
Binary	1	0	1	1
Gray	1	1	1	0

Q2) Write an algorithm for converting from binary to gray code.
You can draw a flow chart.

Index	3	2	1	0
Binary	1	0	1	1
Gray	1	1	1	0

$$\text{Gray}[3] = \text{Binary}[3]$$

$$\text{Gray}[2] = \text{Binary}[2] \text{ XOR } \text{Binary}[3]$$

$$\text{Gray}[1] = \text{Binary}[1] \text{ XOR } \text{Binary}[2]$$

$$\text{Gray}[0] = \text{Binary}[0] \text{ XOR } \text{Binary}[1]$$

